



MIDDLE EAST TECHNICAL UNIVERSITY
Electrical & Electronics Engineering

Simulation Project #3

EE 463

Enes Ayaz – 2093318

Ekin Su Saçın - 2031300



Contents

Introduction	3
1- SPEED CONTROL of DC MOTOR	4
Rectifier Circuit:	4
DC MOTOR:	4
CONROLLING:	4
SIMULATION:.....	5
SIMULATION RESULTS:	6
2- BUCK CONVERTER	7
3-BOOST CONVERTER	11
3.1	11
3.2	12
Simulations:	13
Comments:	15
Conclusion	16
References :	17

Introduction

In this project, we are supposed to drive motor by using thyristor full bridge rectifier, design a buck converter for fixed load at Simulink and design boost converter by using 'Webench' online design tools.

Firstly, Dc motor speed will be controlled by changing firing angle of three phase fully-controlled thyristor rectifiers. The system is closed loop and the speed of motor will be controlled real time. Secondly, a buck converter will be designed. Switching frequency and components will be chosen. Finally, a boost converter will be designed for wanted value of input and output. In addition, a design strategy will be chosen and basis of the strategy will be explained.

In short, AC to DC and DC to DC converter topologies, theoretical information and simulation results will be investigated at the report.

1- SPEED CONTROL of DC MOTOR

In this question, we examined speed control of DC motor by using fully controlled 3-phase thyristor rectifier.

Rectifier Circuit:

3-phase thyristor rectifier are used for obtaining high voltages at output with small ripple. The output voltages are not smooth DC but the voltage ripple is much less than single phase pairs. In addition, the output of rectifier can be controlled by changing the firing angle of thyristors. If the firing angle is smaller than 90 degree, the circuit operates at rectification.

The output voltage formula is stated as:

$$V_o = \frac{3\sqrt{3}}{\pi} \cos(a) V_m (1)$$

V_m is the peak value of line to line voltage and 'a' is the firing angle.

DC MOTOR:

In this part, we used a permanent magnet DC motor. Thus, the dc motor has back-emf constant by considering the field is independent of the motor operations. The motor is loaded by 24 N.m mechanically.

Dc motor can be controlled by armature or field. The motor is controlled by armature control because the motor is permanent magnet and no field control. Speed of the motor is related to back-emf of the motor. However, we do not control directly the back-emf. Thus, we control the terminal voltage to control speed of the motor. The speed control can be closed loop to ensure that the motor speed converges the desired speed. The closed loop is created by directly switch on-off algorithm or combinations of 'PID' controller.

CONROLLING:

The speed of motor is controlled by terminal voltage. The terminal voltage can be adjustable by changing the firing angle. Thus, the speed of motor can be controlled by firing angle. However, the relationship of firing angle and speed is not linear and it is in opposite-relation. In addition, maximum voltage restricts the maximum speed of the motor. The speed of the motor cannot climb over the speed.

SIMULATION:

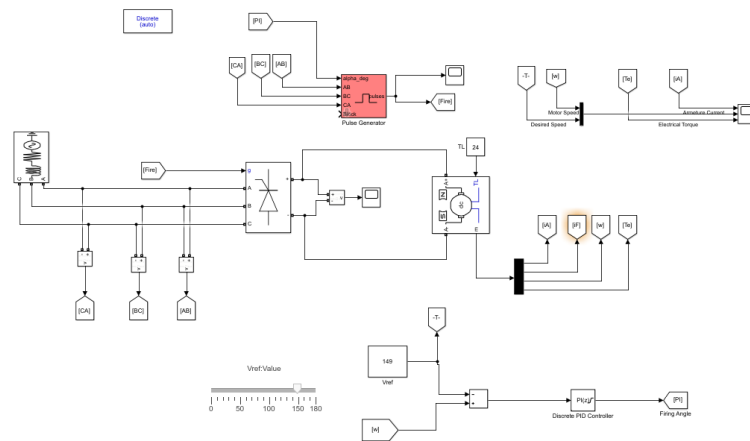


Figure 1 Overall Circuit Diagram of the Speed Control of the DC Motor

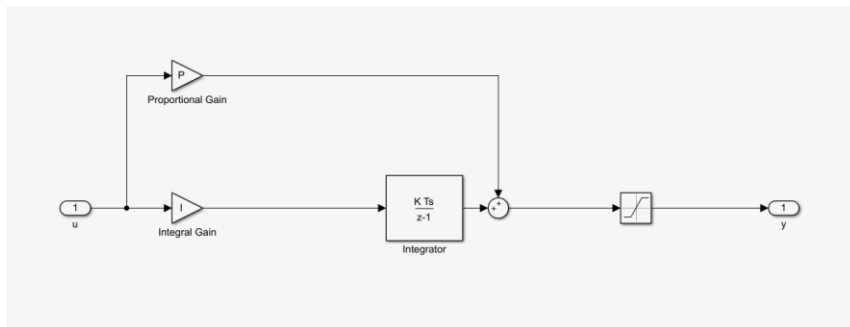


Figure 2 PI Controller

The AC-DC converter and DC motor controlling system are illustrated at Figure 1. The PI controller is illustrated at Figure 2. PI controller has a saturation block because the firing angle is restricted between 0 and 180 degree.

SIMULATION RESULTS:

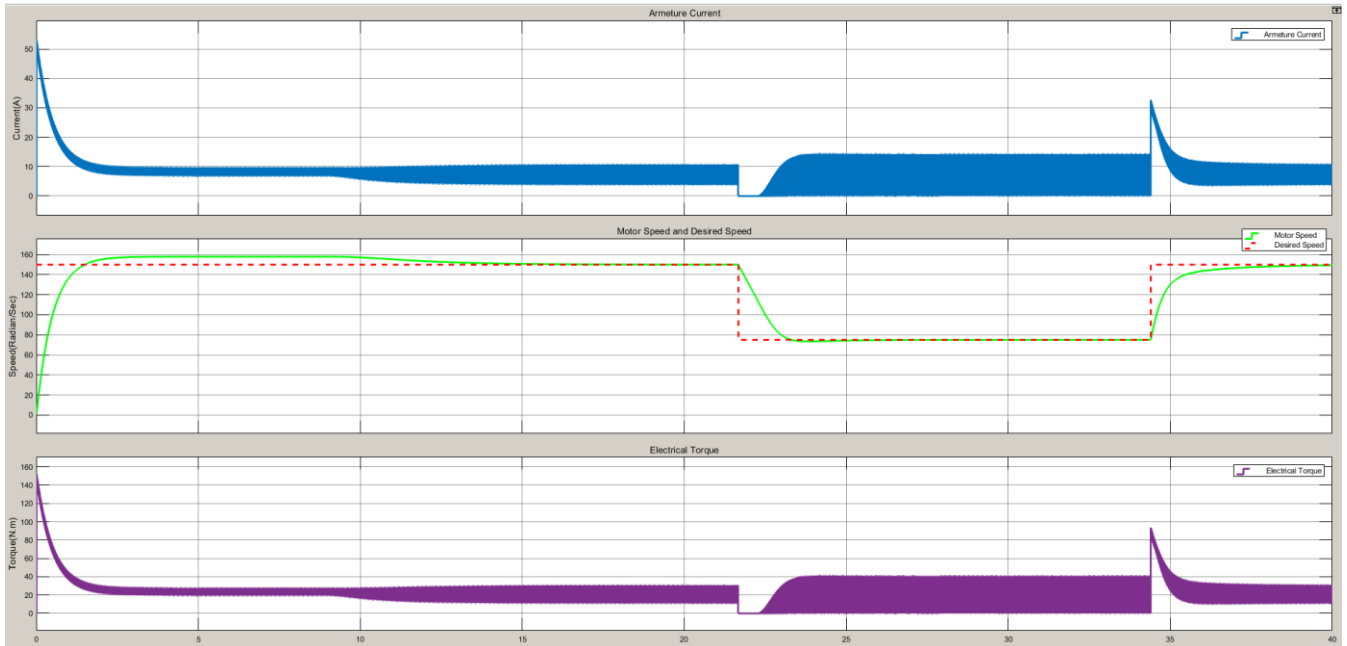


Figure 3 Armature Current ,Motor Speed,,and Electrical Torque with 150 rad/sec and 75 rad/sec Desired Speed

The desired speed is adjusted to 150 rad/sec until the 22 second. The motor maximum speed is 157 rad/sec with restriction of terminal voltage. Thus, the overshoot effect can not be observed at initial. If there was no restriction, overshoot could be observed. For the, 150 rad/sec to 75/rad sec transitions are much smoother than initial because the inertia of the motor was overcome at initially. Thus, there is no overshooting effect at 150 to 75 and 75 to 150 rad/sec transitions at $t=22$ sec and $t=34$ sec.

The desired speed can be increased by slowly. The response of the motor changes.

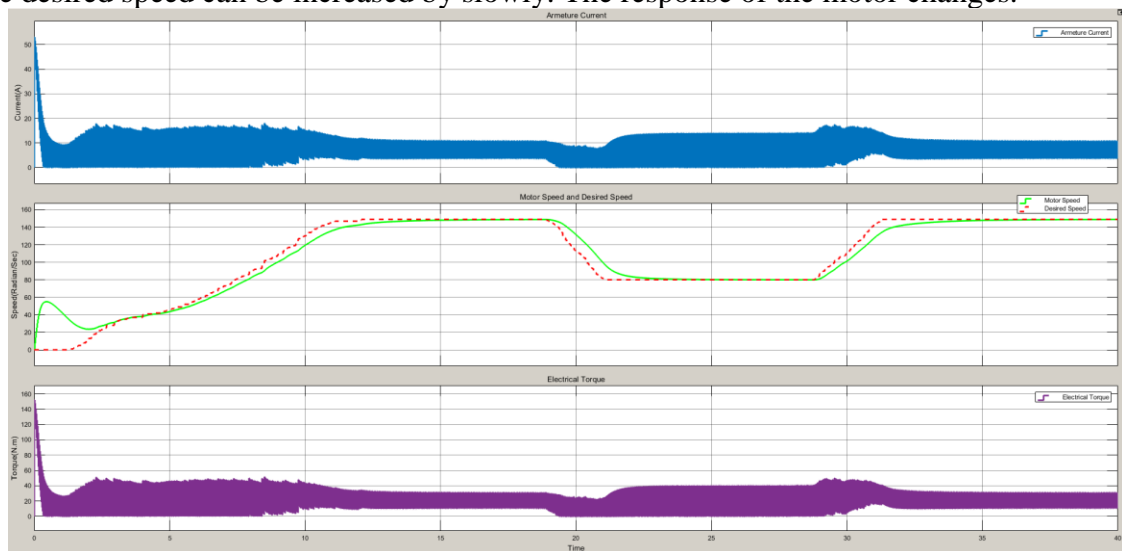


Figure 4 Armature Current ,Motor Speed,,and Electrical Torque with Slowly Changing Desired Speed

The motor speed follows the desired speed narrowly by avoiding abrupt changes at desired speed. Also, the overshoot is observed at initially.

2- BUCK CONVERTER

A buck converter (step-down converter) is a DC-to-DC power converter which steps down voltage (while stepping up current) from its input (supply) to its output (load). Its main application is in regulated dc power supplies and dc motor speed control. Buck converter circuit consists of switching transistor, diode, inductor and capacitor. While the transistor is ON state, current is flowing through the load via inductor and charges the capacitor. While transistor is OFF state, the energy stored in magnetic field around the inductor is released back into the circuit. That back emf from the inductor causes current to flow around circuit via load and diode and charge stored in capacitor becomes the main part of source. In this question, we used a power Mosfet as switch. We used 100 uH inductor and 300 uF capacitor.

$$V_{out}/V_{in} = D$$

D is duty cycle, in this question $D = 28/56=0.5$ which is constant. By varying duty ratio of the switch output voltage can be controlled.

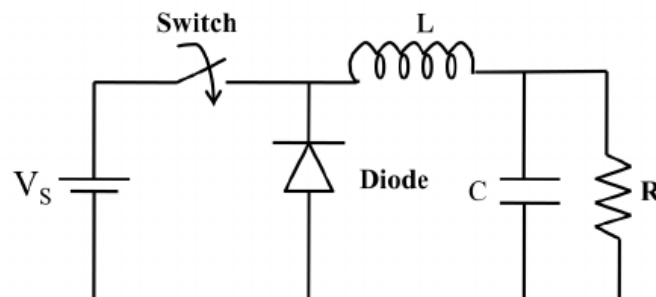


Figure 5 Typical schematic of buck converter

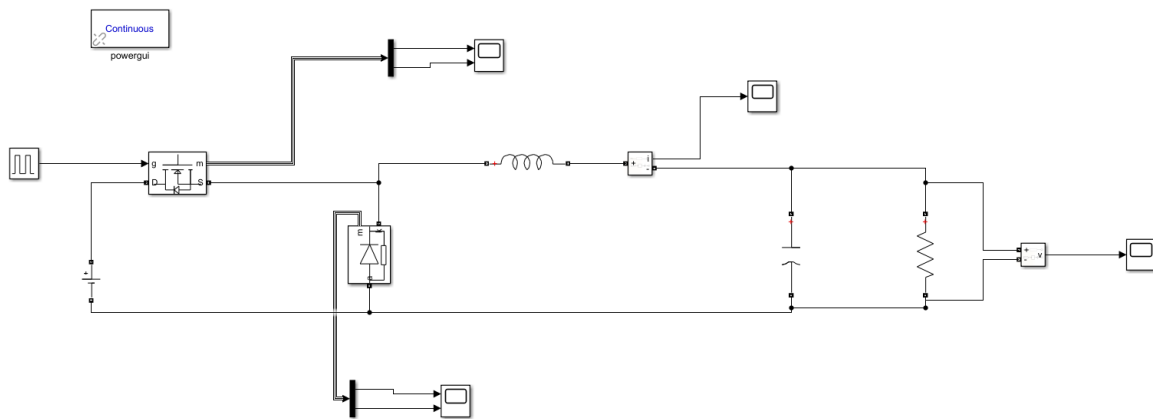


Figure 6 The circuit schematic of designed buck converter

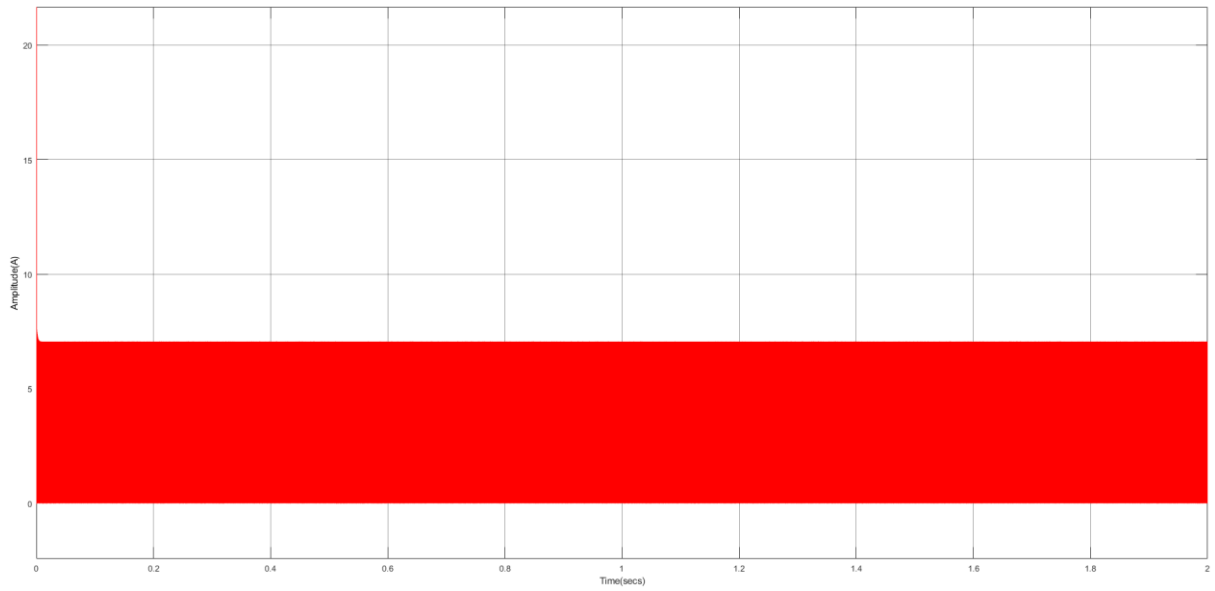


Figure 7 The waveform of IL

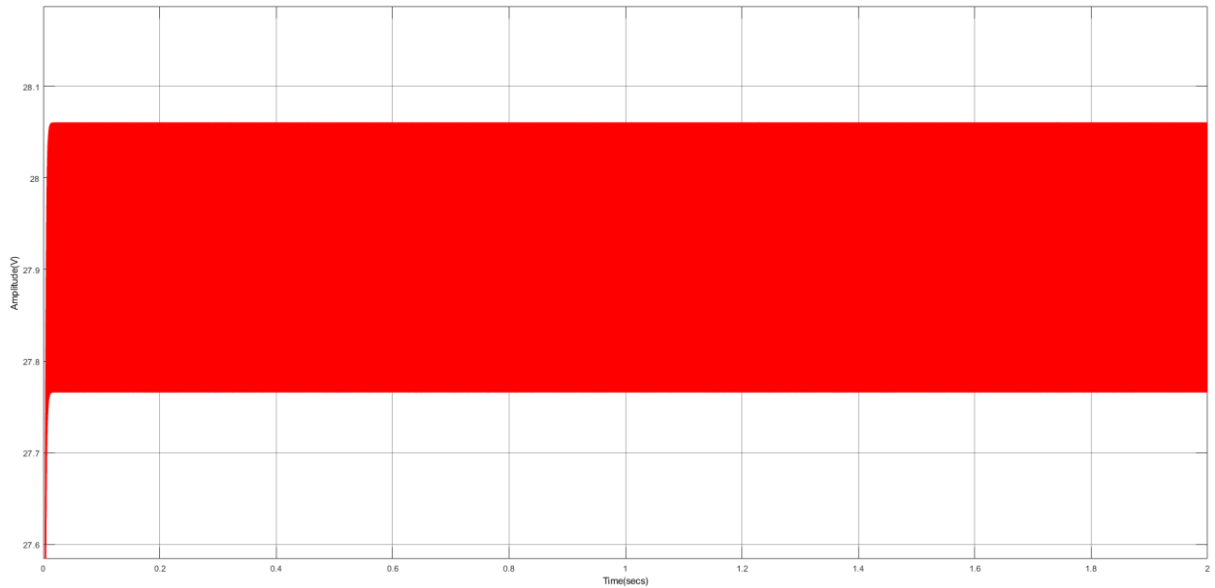


Figure 8 The waveform of Vout

$\Delta V_{out} = 28.06 - 27.767 = 0.293$ from cursor measurements in Simulink. The ripple in the output voltage with a practical capacitor can be calculated by considering the waveforms for continuous conduction operation. The ripple voltage is equal to rate of additional charge and capacitance value. Assuming that all of the ripple component in i_L flows through the capacitor and its average voltage component flows through the load resistor, area between peak of i_L and I_o gives the additional charge.

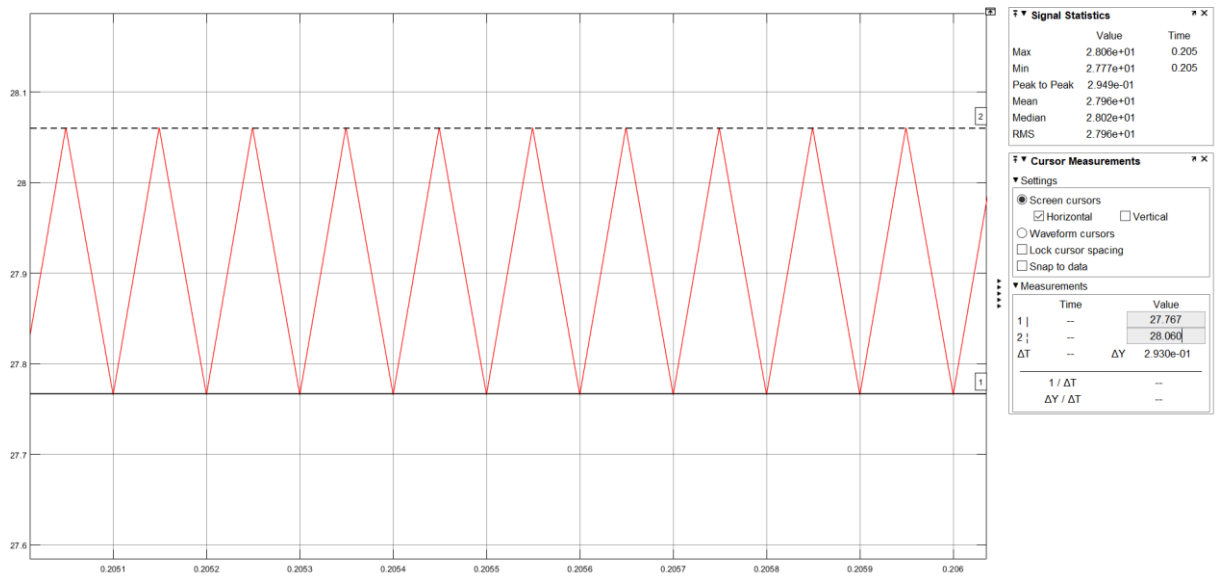


Figure 9 The cursor measurement and signal statistics for ripple voltage

$\Delta IL = 7$ from cursor measurement in Simulink.

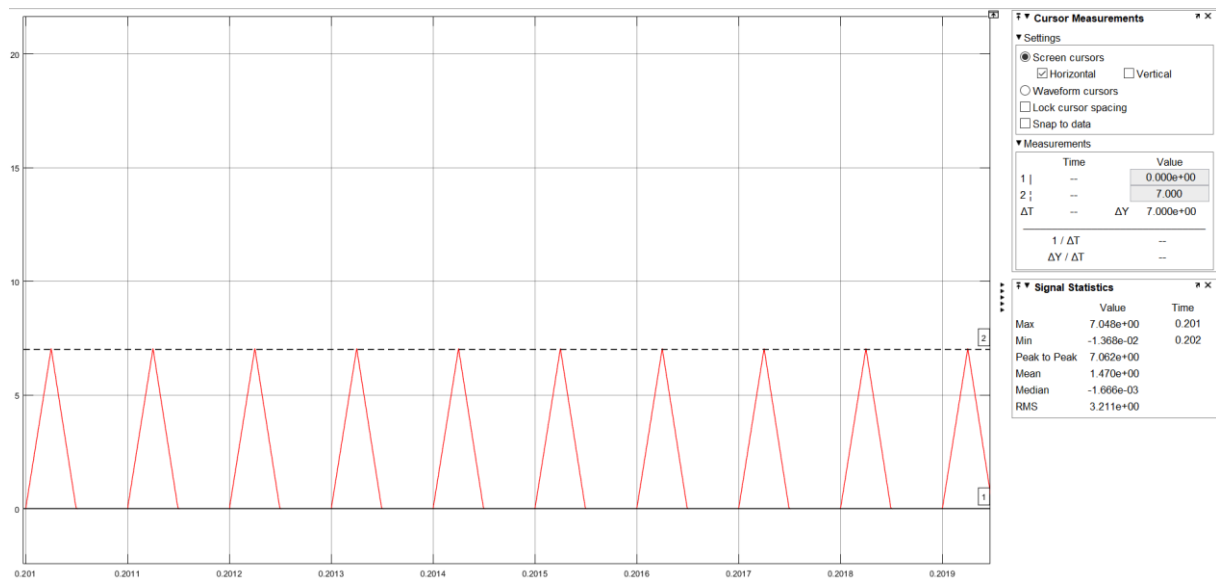


Figure 10 The cursor measurement and signal statistics for ΔIL

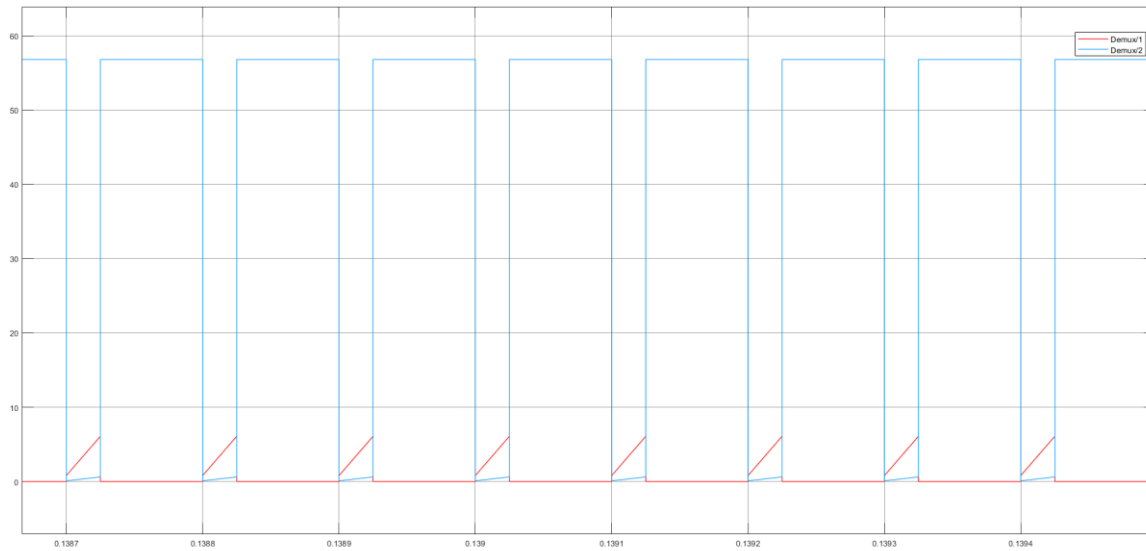


Figure 11 The waveform of current through mosfet (I_{fet})

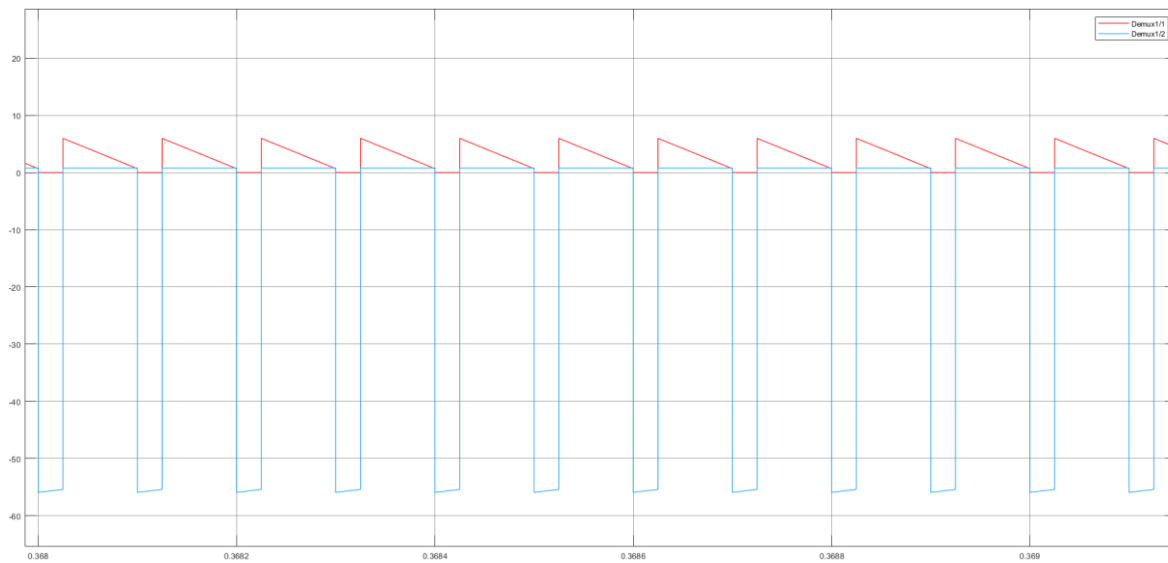


Figure 12 The waveform of current through diode (I_d)

While designing the buck converter, we chose the components which we used from [2] with corresponding payment and manufacturer part no as seen in Table 1.

Component	Cost	Mfr. Part No
4 Ω resistor	1.32 €	CW02B4R000JE12
Power mosfet	7.82 €	SIHG47N60AEF-GE3
Diode	1.49 €	RFN20TF6SFHC9
100 μ H inductor	2.62 €	SPM7054VT-101M-D
300 μ F capacitor	2.18 €	EGPA101ELL301ML25S

Total cost: 15.43 €

Table 1- Cost and Mfr. Part No of components of buck converter

3-BOOST CONVERTER

A boost converter is step-up converter that increases the voltage (while decreasing the current). The converters have basically at least two semiconductors (2 Mosfets or 1 diode and 1 Mosfet) to switch. Also, it has energy storage elements such as capacitor and inductor. The energy storage elements can be used for filtering the output.

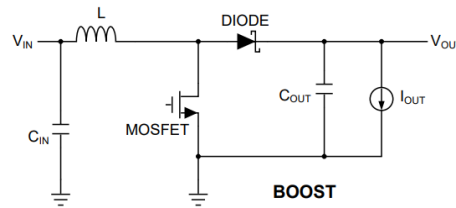


Figure 53 Basic Circuit of Boost Converter [1]

Diode can be replaced by a Mosfet and it is called synchronous boost converter. Diode on resistance is bigger than mosfets on resistance in general. Thus, the synchronous boost converter is more efficient.

3.1

Figure 14 Input and Output of the Boost Converter

Figure 2 illustrates the input and output relations of the converter.

The Power Designer gives some selection about design consideration. I chose the 'high efficiency' design because the efficiency affects the other parameters indirectly. For example, power loss is determined by efficiency and it affects thermal cooling.

For the advanced selection:

Regulator Type: Converter (Integrated Switch)

Design Attributes:

Efficiency: %90-98

BOM Cost: 3-5 Dollars

BOM Area: 191-578 (mm²)

Switching Frequency: 300-500 (kHz)

Inductor Ripple current: 0-1.6 (A)

Crossover Frequency: 1-33 (kHz)

Phase Margin: 24-68 (°)

BOM Count: 16-44

Topology: Boost

IC Features: Frequency Synchronization

My design is based on high efficiency, low-power dissipation and high power density because that the features are figure of merit of any design. The cost can be added to them.

3.2

I chose TPS61088-Q1

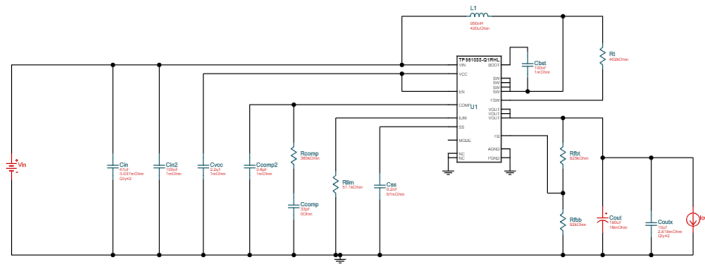


Figure 15 The Circuit Schematic of the Bus Converter

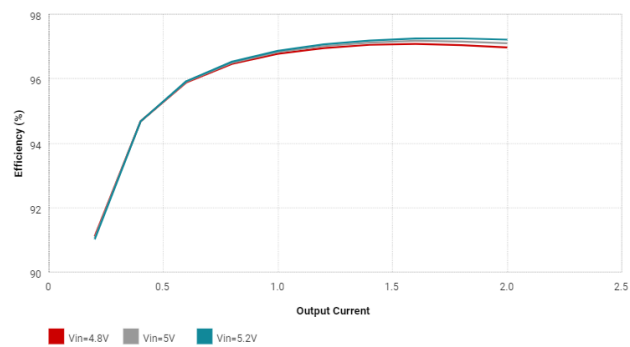


Figure 16 Efficiency vs Output Current Graph

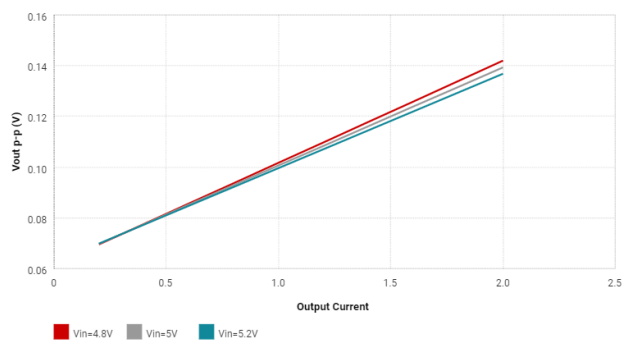


Figure 17 Output Voltage Ripple vs Output Current Graph

Inductor Current Peak to Peak Value	7.74 A
Output Voltage Peak to Peak Value	141.96 mV
Efficiency	%97
IC Junction Temperature	49.43
Mode	BOOST CCM
Footprint	394 mm^2
BOM Cost	5.26 Dollars

Table 2: Table of Some Operation Properties

Cin Pd	7.59 mW	Power	Input capacitor power dissipation
Cout Pd	56.66 mW	Power	Output capacitor power dissipation
L Pd	13.03 mW	Power	Inductor power dissipation
IC Pd	671.04 mW	Power	IC power dissipation
Coutx Pd	1.38 mW	Power	Output capacitor_x power loss
Total Pd	749.92 mW	Power	Total Power Dissipation

Table 3: Power Loss of all Components

Simulations:

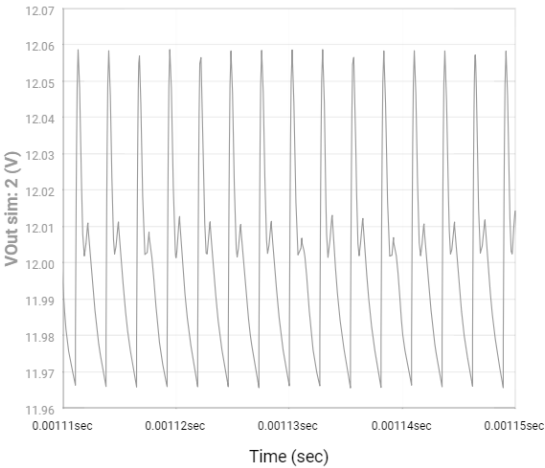


Figure 18 Output Voltage vs Time Graph for Steady-State

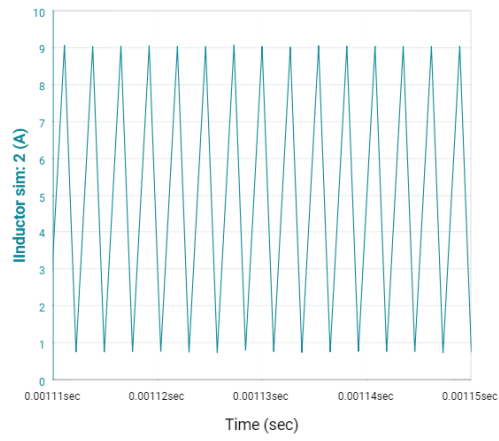


Figure 19 Inductor Current vs Time Graph for Steady-State

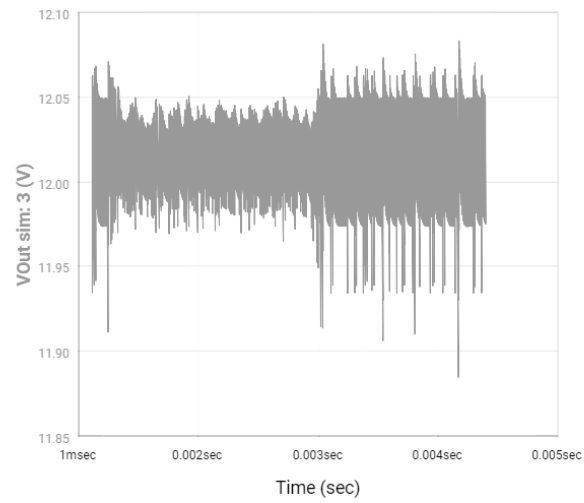


Figure 20 Output Voltage vs Time for Load Transient

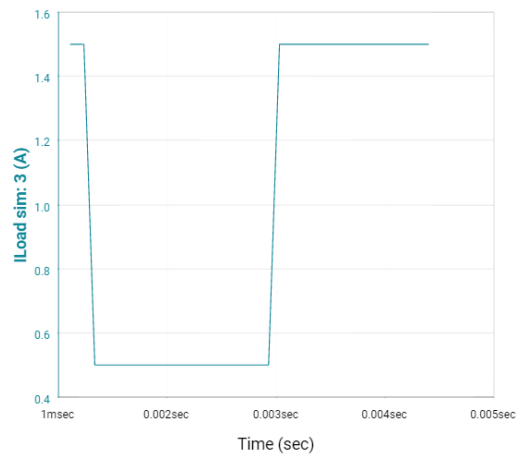


Figure 21 Load Current vs Time for Load Transient

Comments:

Firstly, we examined the efficiency and output voltage ripple in respect to different output current at Figure X and X+1. It was observed that output ripple increases while the output current increases. However, the ripple is very small and negligible for all of current until 2 Amperes (Rated Power). The efficiency is low when the converter is at discontinues mode, the output current is low.

Secondly, our design is based on low power loss, high efficiency. Table 1 and 2 shows that the design provides them. Efficiency is % 97.

Finally, there are 4 simulation results which are steady-state output voltage, steady state inductor current and transient load voltage and current.

Steady state output voltage is almost purely DC. It swings between 11.97 and 12.06. Voltage ripple is low and the converter works properly at steady state.

Steady state inductor current shows that the inductor charges for the time without connection of load. Then, the charges flow the load when connection of load starts and the inductor current decreases.

As thinking about the basic asynchronous boost converter:

DT:

$$\frac{di_L}{dt} = \frac{V_{in}}{L} \quad (2)$$

(1-D)T :

$$\frac{di_L}{dt} = \frac{V_{in}-V_{out}}{L} \quad (3)$$

For the transient of the load, the output voltage was increasing to 12 volt fastly and swings. The load current is smaller for the transient time. However, transition time is small, it passes the steady-state 1 msec.

Conclusion

. In this report, AC-DC application and DC-DC topologies are argued. Methods of closed loop speed control of DC motor by thyristor rectifier were investigated. DC-DC buck and boost converter topologies are simulated.

Effect of the firing angle was observed for the output voltage of rectifier circuit. Speed control of dc motor are argued and the armature control was used by PI controller.

Buck converter and output characteristic were investigated. Load of the buck converter is constant, so the there is no required closed loop controlling. The ripple of output voltage was observed and filter required for the avoiding switching harmonics were designed.

Boost converter were designed by using tools by TI. The design requirements are chosen to provide high efficiency and high-power density.

In short, design requirements for different topologies and their importance are investigated. In addition, it is experimented how to emphasize on some features while neglect some.

References :

- [1] Stasi, F. Working with Boost Converters. Retrieved from Texas Instruments website: <http://www.ti.com/lit/an/snva731/snva731.pdf>
- [2] Mouser.com.tr. (2019). *Mouser Electronics Turkey - Electronic Components Distributor*. [online] Available at: <https://www.mouser.com.tr/> [Accessed 6 Jan. 2019].